



OSCILLOQUARTZ

SWATCH GROUP ELECTRONIC SYSTEMS

Quartz Crystal Oscillators and Phase Locked Loops

Dominik Schneuwly

Yves Schwab



Content

1. Quartz Crystal Resonator Technology
 - ❖ Quartz, crystal lattice and piezo-electric effect
 - ❖ Vibration modes and equivalent circuit
 - ❖ Cuts
 - ❖ Ageing mechanisms
2. Quartz Crystal Oscillator (XO) Technology
 - ❖ TCXO
 - ❖ MCXO
 - ❖ OCXO
 - ❖ DOCXO
3. XO Performance vs. Telecom Requirements
 - ❖ Frequency holdover
 - ❖ Phase holdover
4. Phase Locked Loops (PLL)



OSCILLOQUARTZ

SWATCH GROUP ELECTRONIC SYSTEMS

1. Quartz Crystal Resonator Technology




Quartz Crystal

Quartz = SiO_2

Pink = silicon atoms

Blue = oxygen atoms


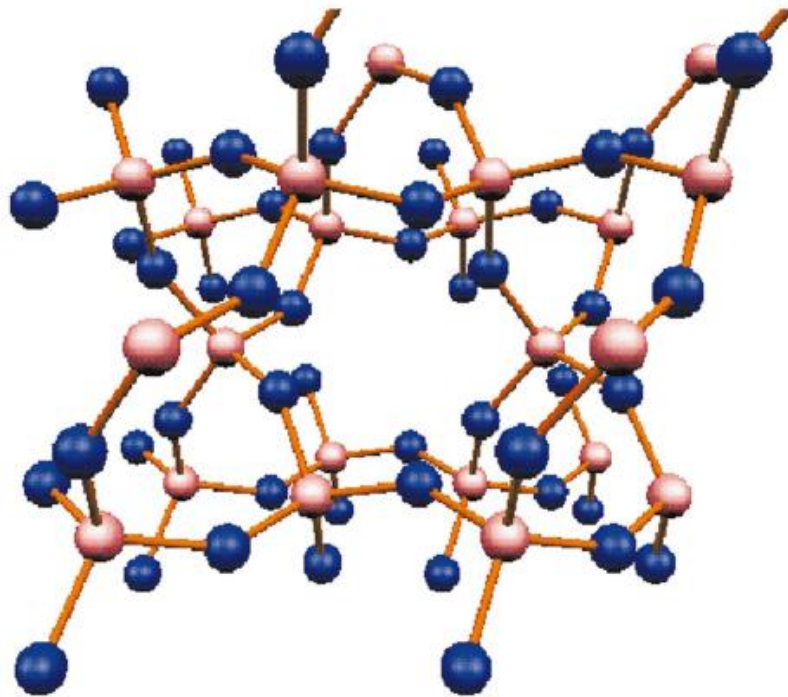


Quartz lattice




Cuts

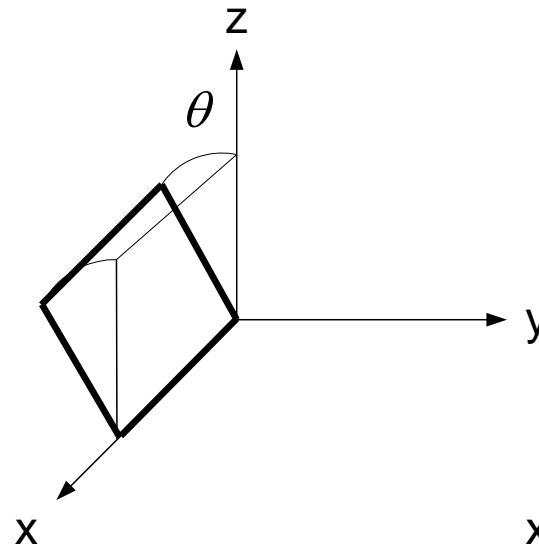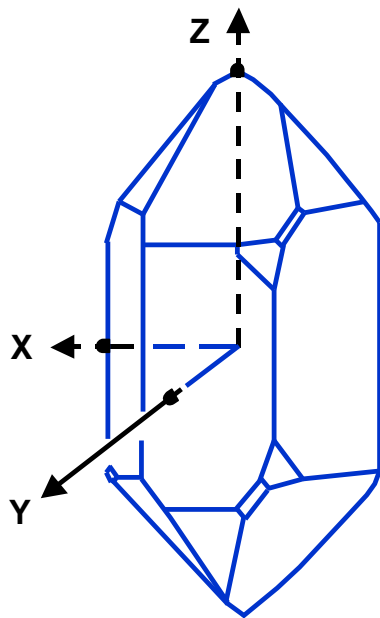Small disks are cut out of the crystal at given angles.



**Single rotated cut
(e.g. AT-cut)**

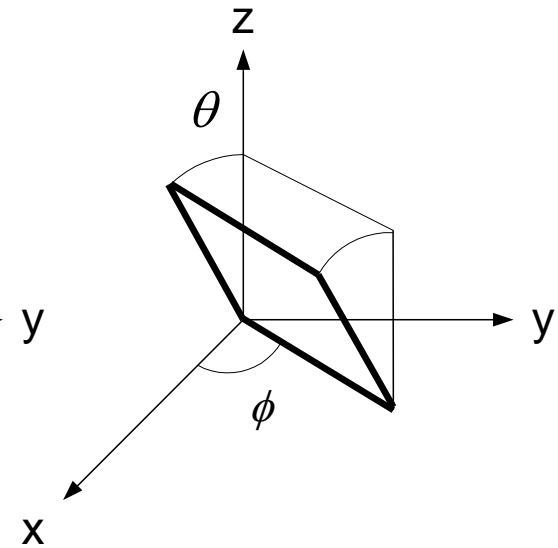


**Double rotated cut
(e.g. SC-cut)**




Cuts

Angle accuracy: $\pm 10''$ (for SC-cut)

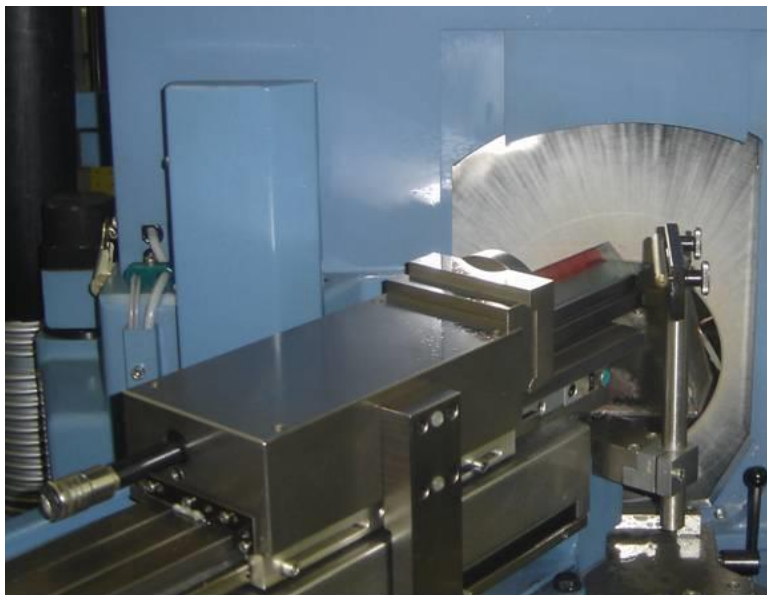





Vibration Modes

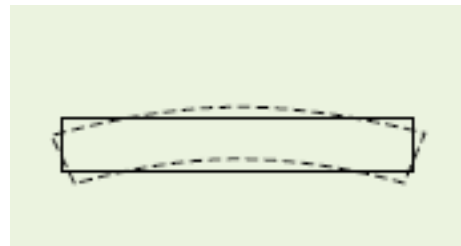


Flexure Mode

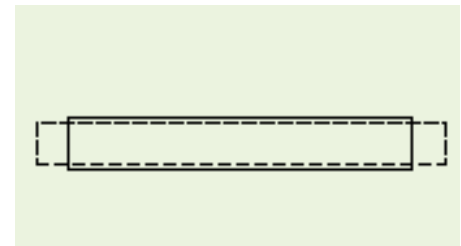


Extensional Mode

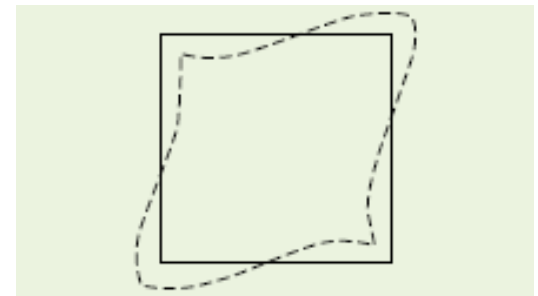


Face Shear Mode

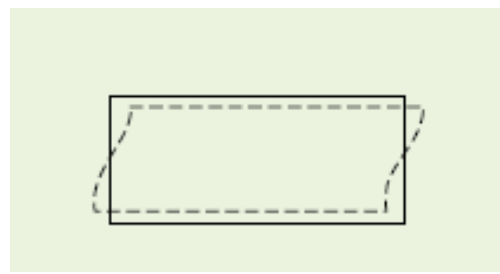

Thickness Shear Mode

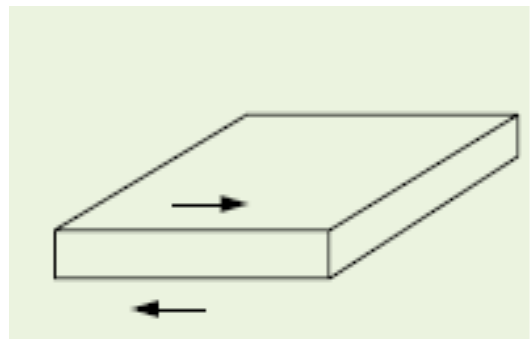

Fundamental Mode Thickness Shear

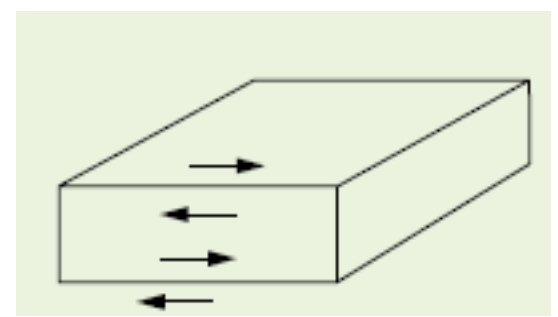


Third Overtone Thickness Shear



Piezo-electric Effect


Piezo-electric effect:

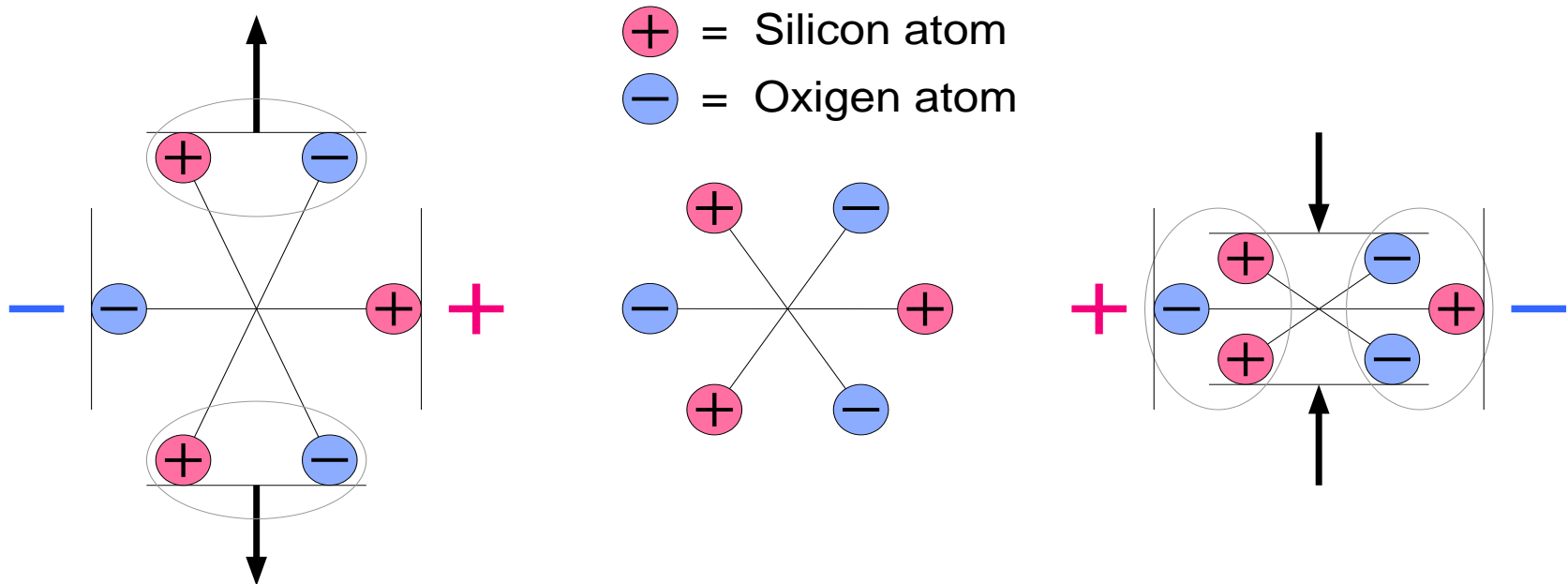- Mechanical strain \Rightarrow voltage
- Voltage \Rightarrow mechanical deformation






Piezo-electric Effect

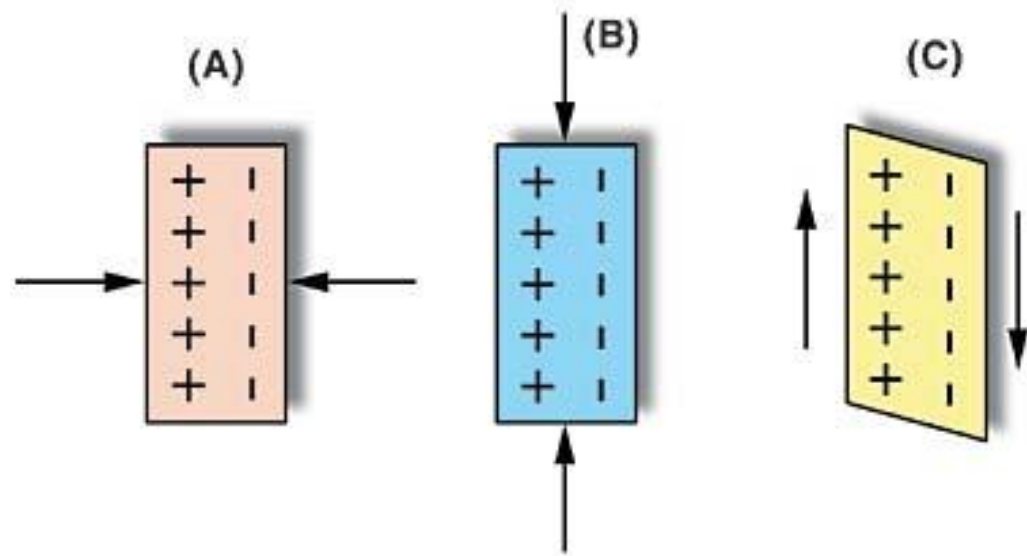

Strain Axis	Field Axis & Mode		
	(A)	(B)	(C)
x	x		x
y		x	y
z			y




Equivalent Circuit

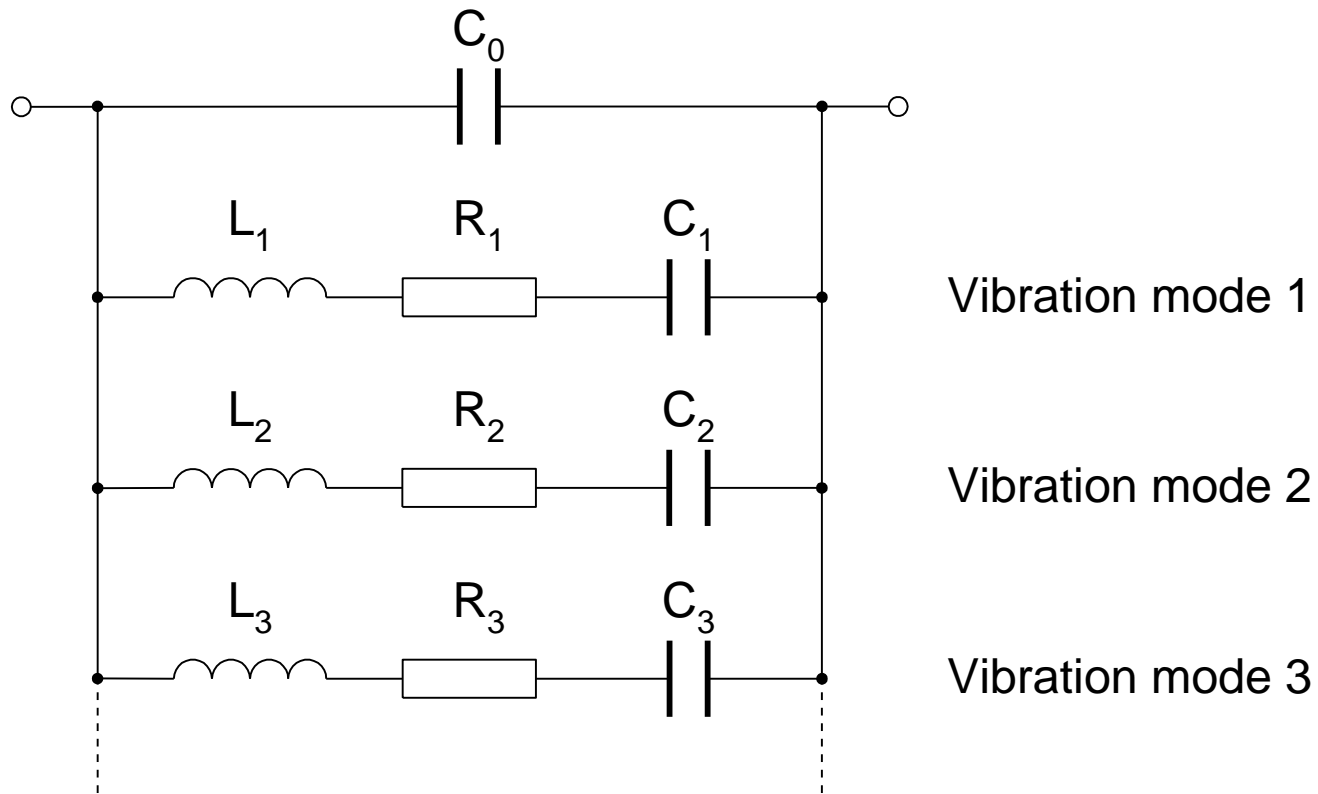




Admittance $Y(f)$

$|Y(f)|$

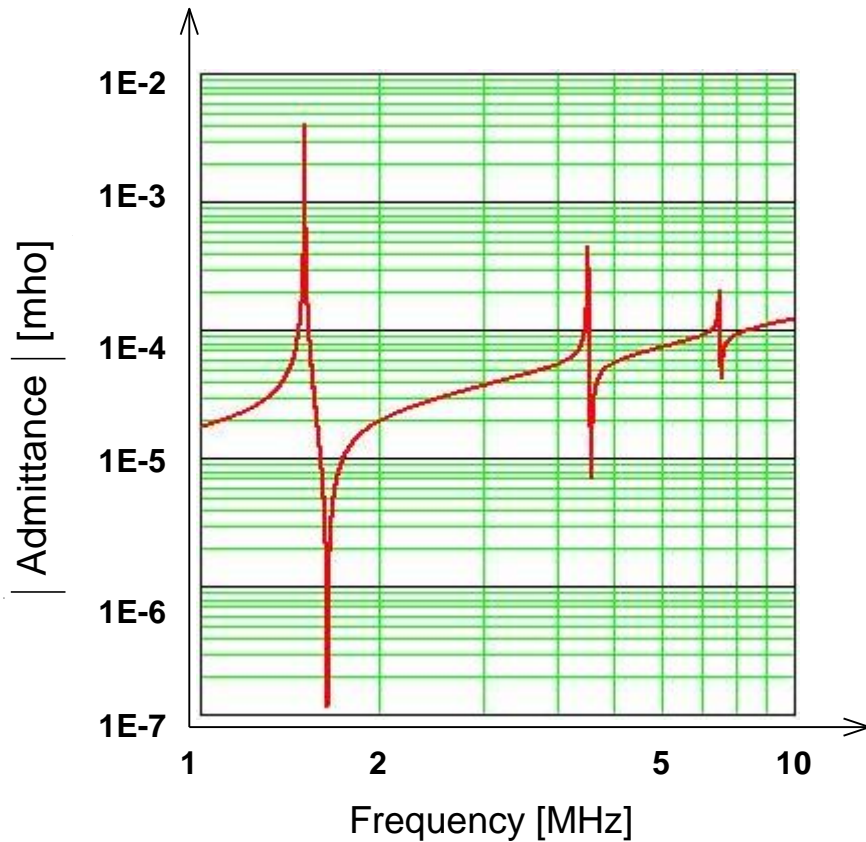


$\text{Arg}(Y(f))$

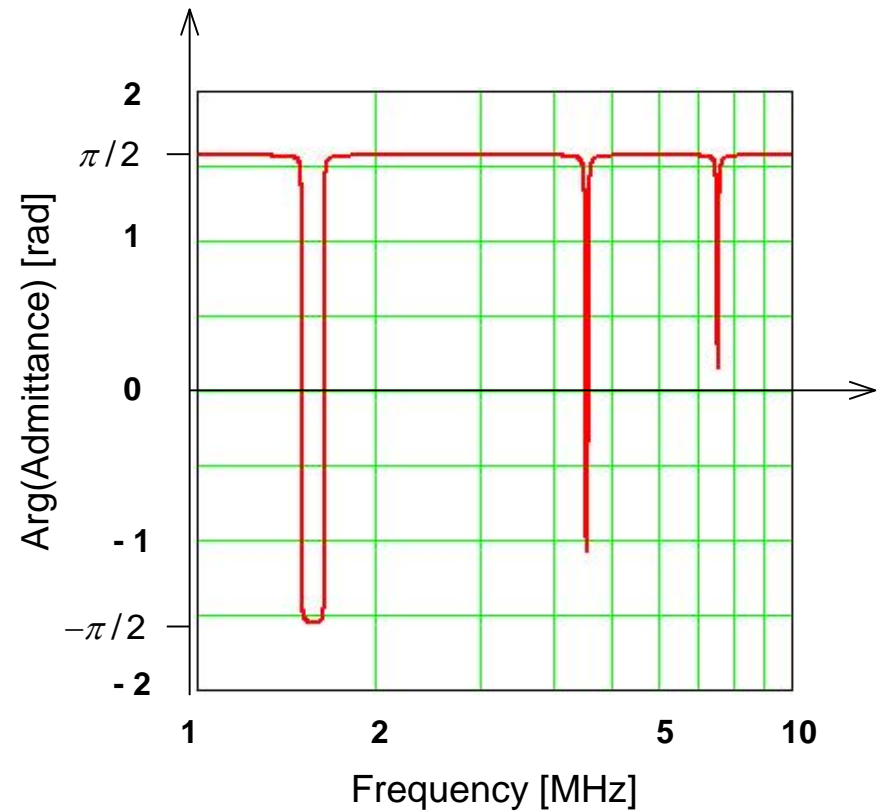

Note: Exaggerated resistance values R_1 , R_2 and R_3 for better readability



Quartz Crystal Oscillator (XO)

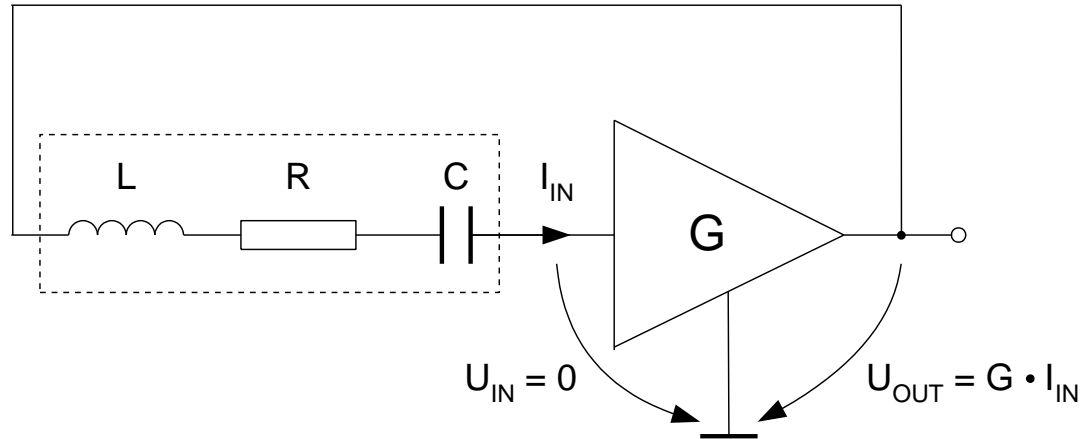


$$\text{Open Loop Gain: } H(\omega) = G \cdot Y(\omega) = \frac{G}{j \cdot \omega \cdot L + R + \frac{1}{j \cdot \omega \cdot C}}$$

$$\text{If } G = \frac{1}{R} \text{ and } \omega = \omega_0 = \frac{1}{\sqrt{L \cdot C}} \text{ then } H(\omega = \omega_0) = 1$$

$$f_0 = \frac{\omega_0}{2 \cdot \pi} = \text{resonance frequency}$$



Frequency Drift Due to Ageing

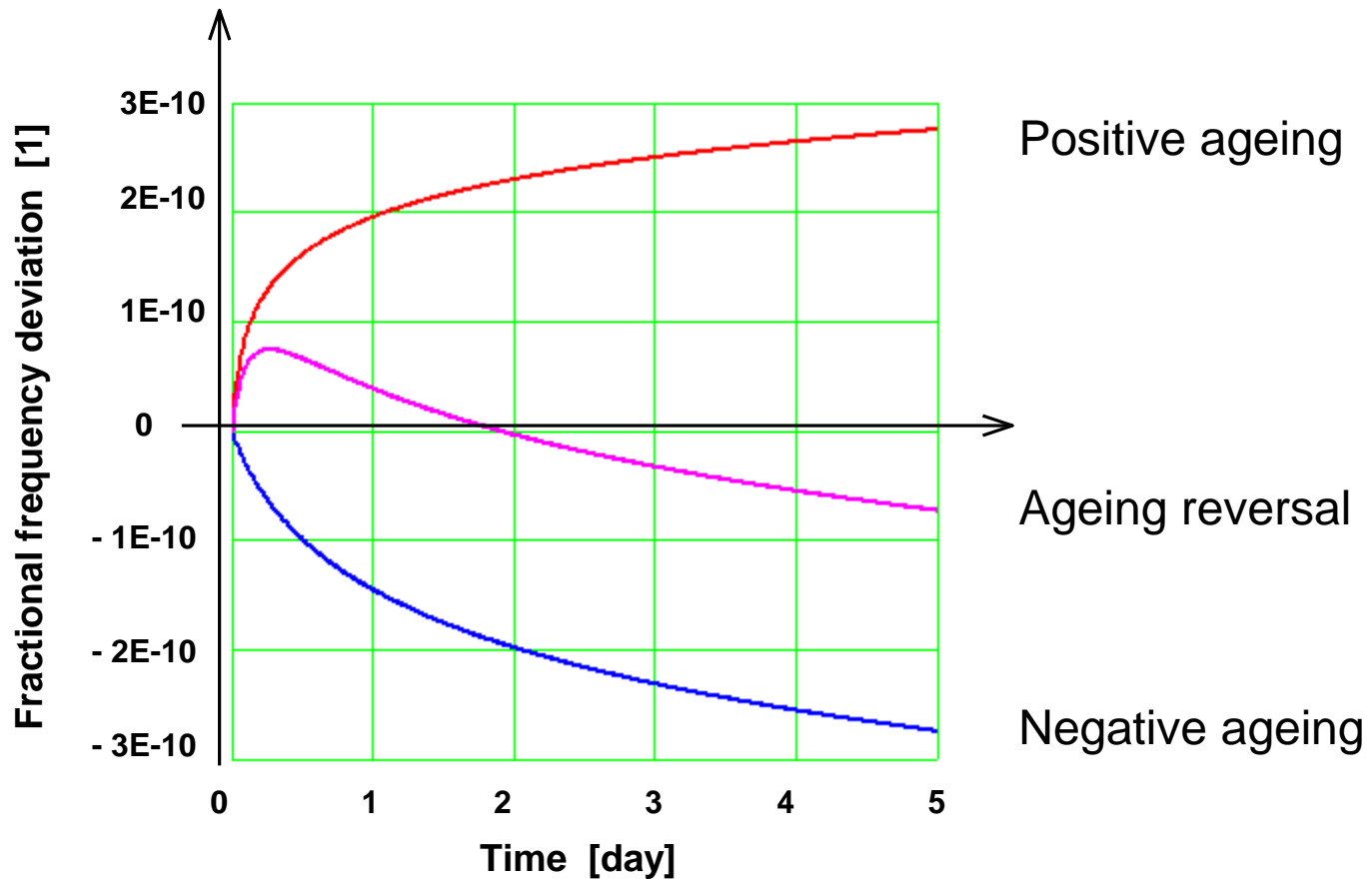




Ageing Mechanisms

- Mass transfer due to contamination (e.g. electrode metal atoms into the crystal)
- Stress relief in the resonator's mounting and bonding structure, electrodes, and in the quartz
- Other mechanisms:
 - ❖ Quartz outgassing
 - ❖ Diffusion effects
 - ❖ Chemical reaction effects
 - ❖ Pressure changes in resonator enclosure (leaks and outgassing)
 - ❖ Oscillator circuit aging (load reactance and drive level changes)
 - ❖ Electric field changes (doubly rotated crystals only)
 - ❖ Oven-control circuitry aging



BVA Resonator

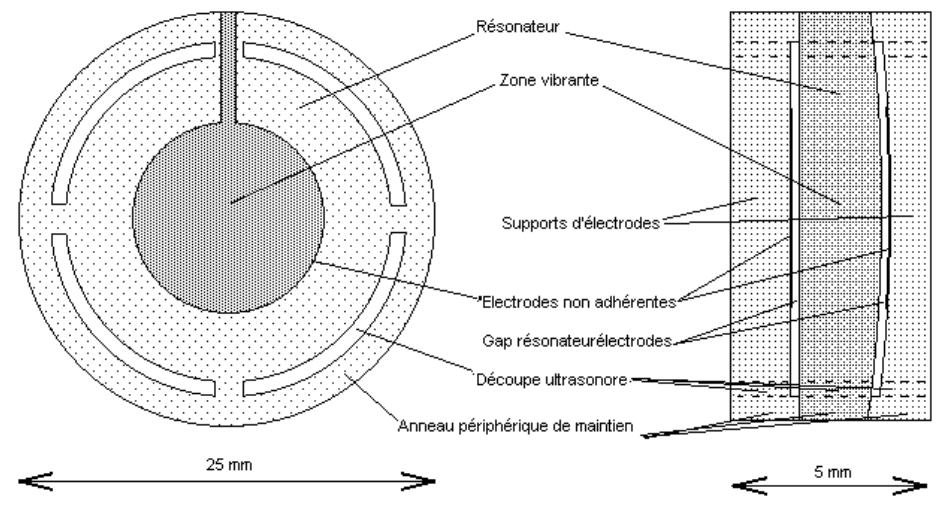- Electrodes not in direct contact with the resonator body \Rightarrow contamination of the resonator body is stopped \Rightarrow
- Ageing improves by a factor of 10 or more
- Other performance parameters improve also (Q, temperature sensitivity, phase noise, etc.)



Courtesy Jean-Pierre Aubry




AT-cut Resonator

AT-cut:

- $\Theta = 35^\circ$
- $\Phi = 0$

$\Delta f/f$ as a function of temperature
(parameter: $\Delta\Theta$ = deviation from reference angle)

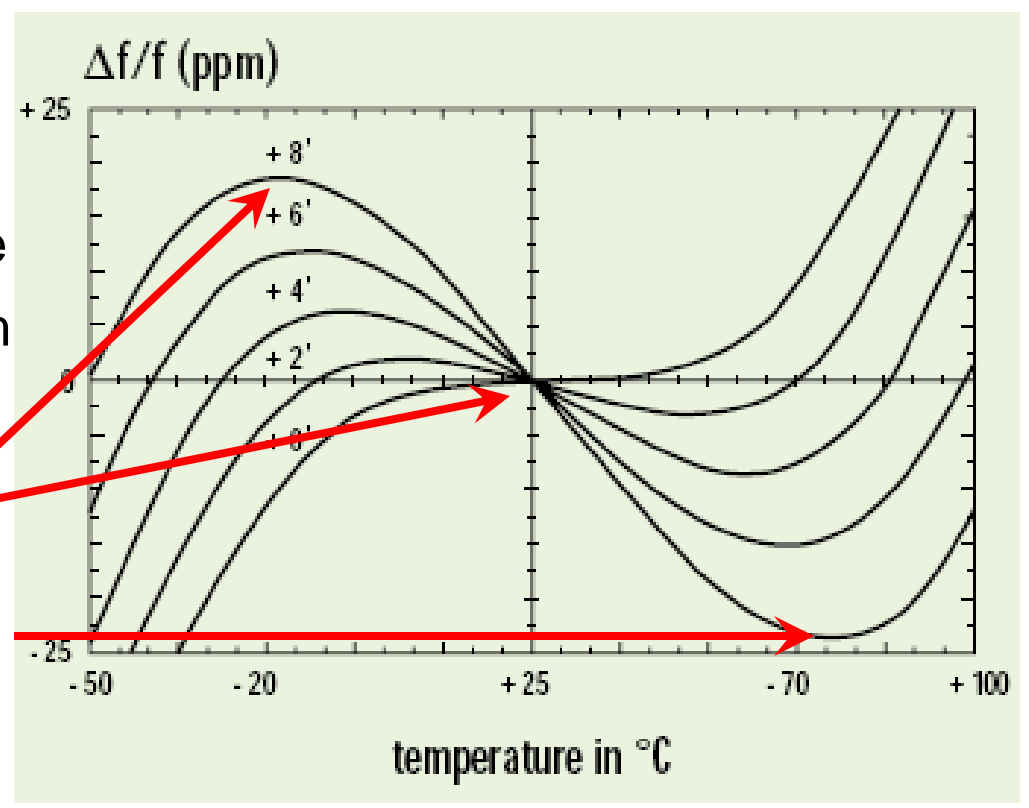- Lower Turnover Point (LTP)
- Inflection Point (IP)
- Upper Turnover Point (UTP)






SC-cut Resonator

SC-cut:

- $\Theta = 34^\circ$
- $\Phi = 22^\circ$

$\Delta f/f$ as a function of temperature
(parameter: $\Delta\Theta$ = deviation from reference angle)

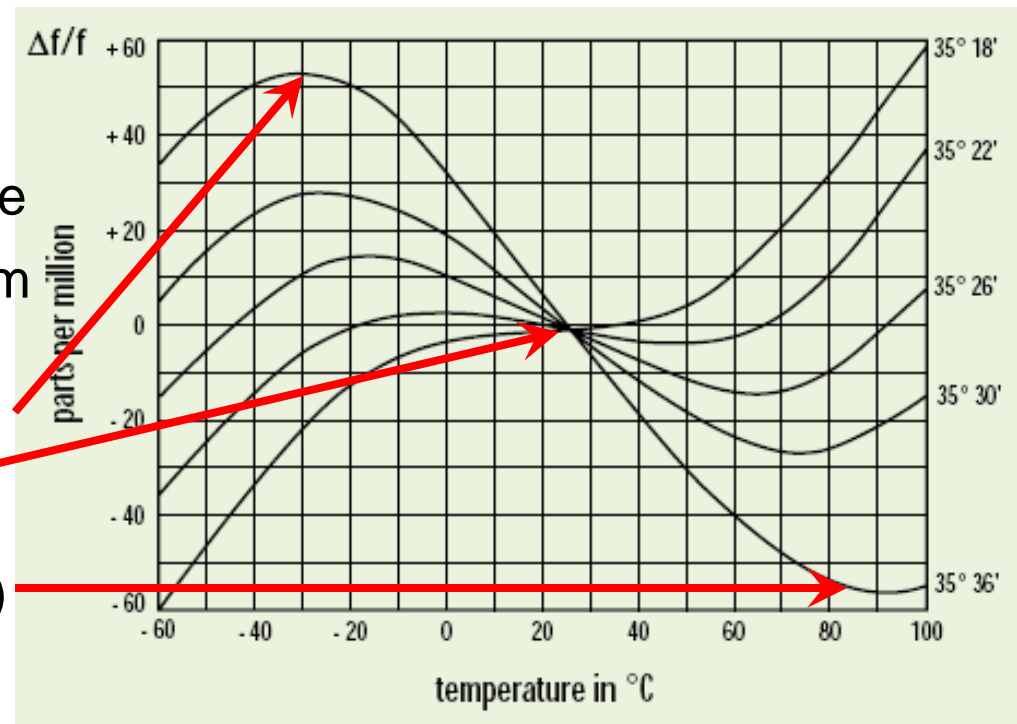- Lower Turnover Point (LTP)
- Inflection Point (IP)
- Upper Turnover Point (UTP)





SC- versus AT-cut

Advantages of the SC-cut

- Thermal transient compensated (allows faster warm-up OCXO)
- Static and dynamic $f(T)$ allow higher stability OCXO
- Planar stress compensated; lower Δf due to edge forces and bending
- Better $f(T)$ repeatability allows higher stability OCXO (less Δf for oscillator reactance changes)
- Lower drive level sensitivity
- Higher Q for fundamental mode resonators of similar geometry
- Higher capacitance ratio (less Δf for oscillator reactance changes)
- Less sensitive to plate geometry - can use wide range of contours
- Far fewer activity dips
- Lower sensitivity to radiation

Disadvantages of the SC-cut

- More difficult to manufacture



OSCILLOQUARTZ

SWATCH GROUP ELECTRONIC SYSTEMS


2. Quartz Crystal Oscillator (XO) Technology



XO Categories rel. Temp. Control

XO, Crystal Oscillator:

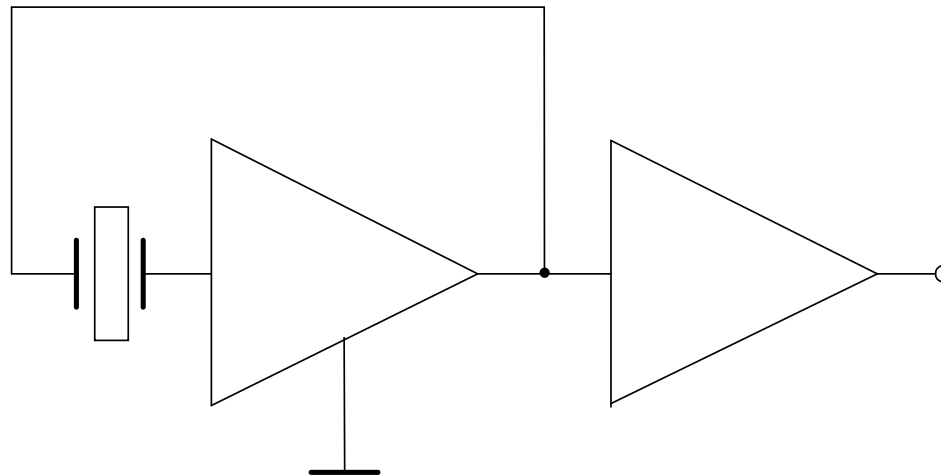- LTP centered in the operation temperature range
- $> 1E-7 / ^\circ\text{C}$






XO Categories rel. Temp. Control

TCXO, Temperature Compensated XO:

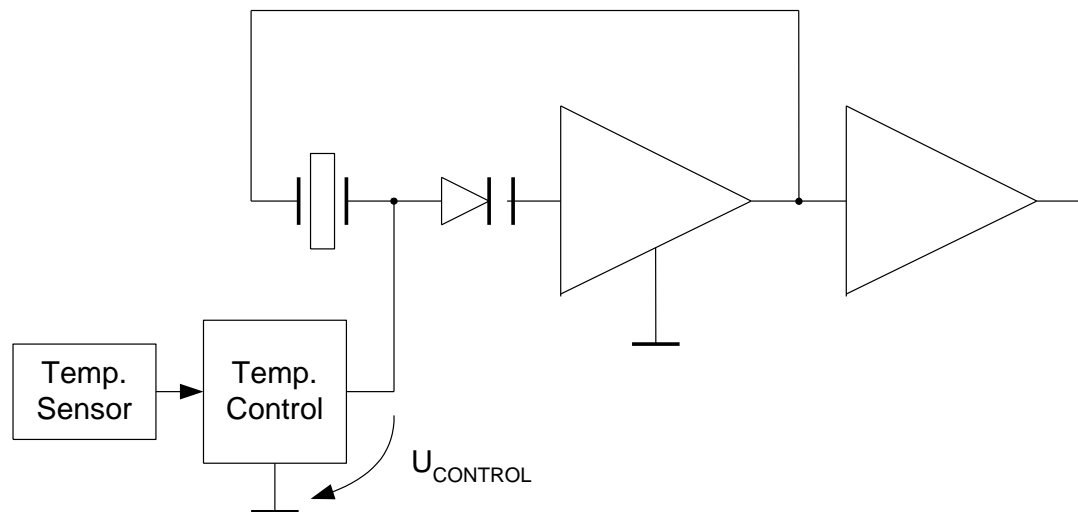- Resonance frequency is modified by a varactor diode so as to compensate temperature sensitivity
- $5E-8$ to $5E-7$ over $[-55^{\circ}\text{C}$ to $85^{\circ}\text{C}]$






XO Categories rel. Temp. Control

MCXO, Microcomputer Compensated XO:

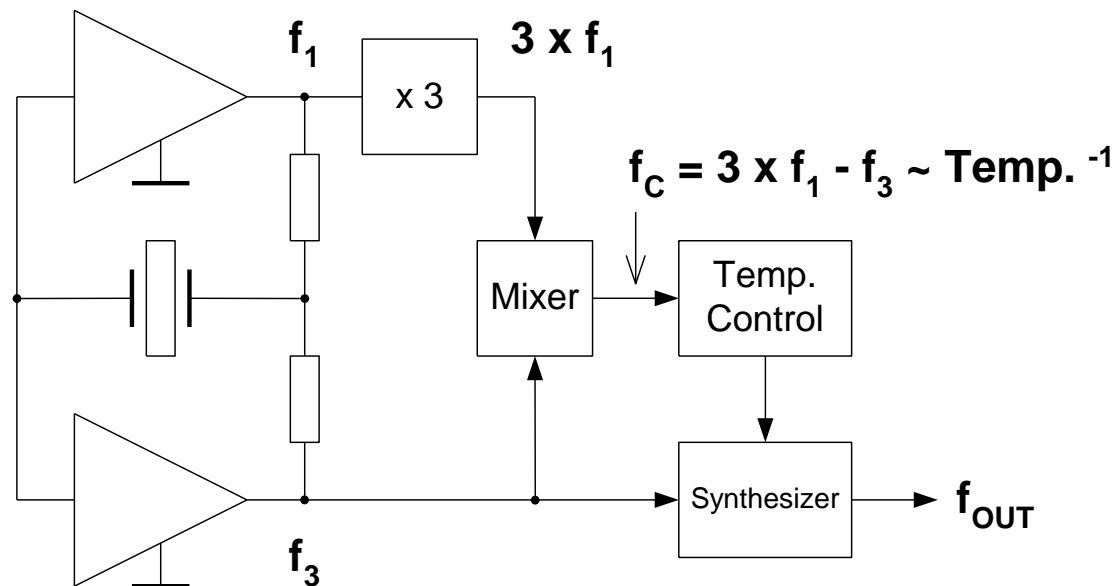- Dual mode oscillator generating fundamental (f_1) and third overtone (f_3).
- Difference between f_3 and $3 \times f_1$ is used to measure temperature and compensate temperature sensitivity of f_3 .






XO Categories rel. Temp. Control

OCXO, Oven Controlled XO:

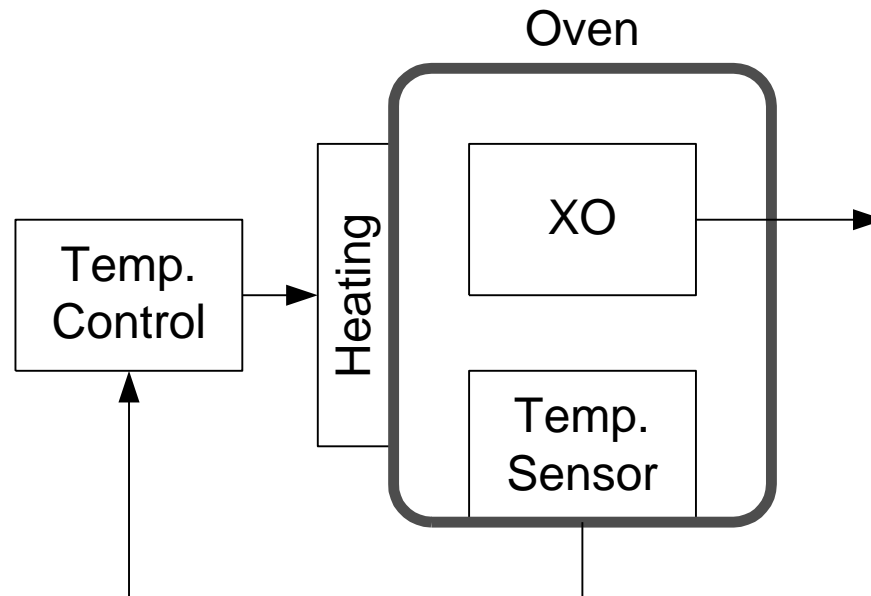- A control loop maintains the oven containing the XO at (nearly) constant temperature.
- $5E-9$ to $5E-8$ over $[-30^{\circ}\text{C}$ to $60^{\circ}\text{C}]$






XO Categories rel. Temp. Control

DOCXO, Double Oven Controlled XO:

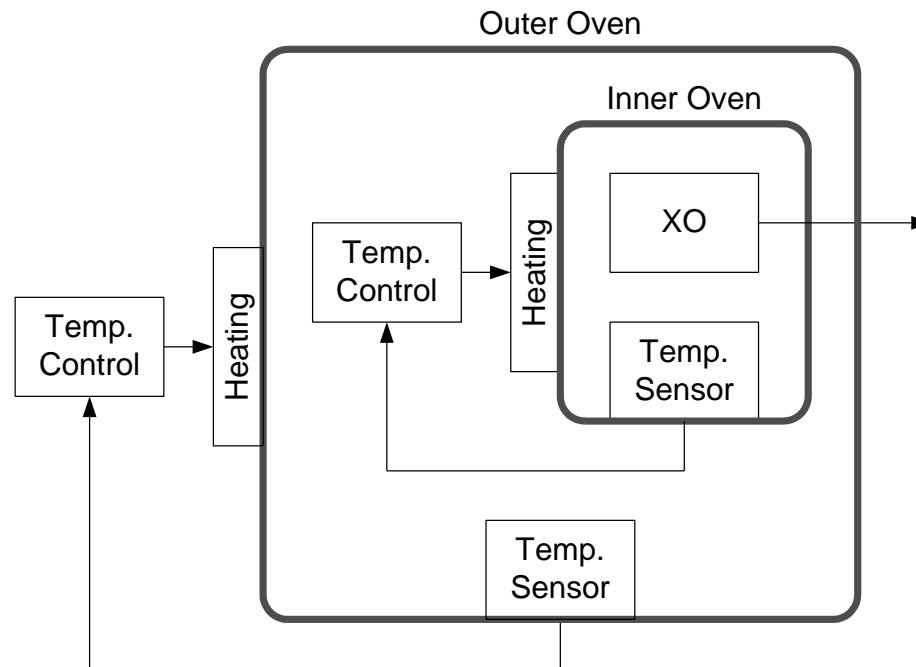- Two temperature controlled ovens, one inside the other.
- $2E-10$ to $5E-9$ over $[-30^{\circ}\text{C}$ to $60^{\circ}\text{C}]$
- BVA resonator: $1E-10$ over $[-30^{\circ}\text{C}$ to $60^{\circ}\text{C}]$, $5E-11$ over $[-15^{\circ}\text{C}$ to $60^{\circ}\text{C}]$





Typical XO's

SOCXO:



DOCXO:



BVA-DOCXO:





OSCILLOQUARTZ


SWATCH GROUP  ELECTRONIC SYSTEMS

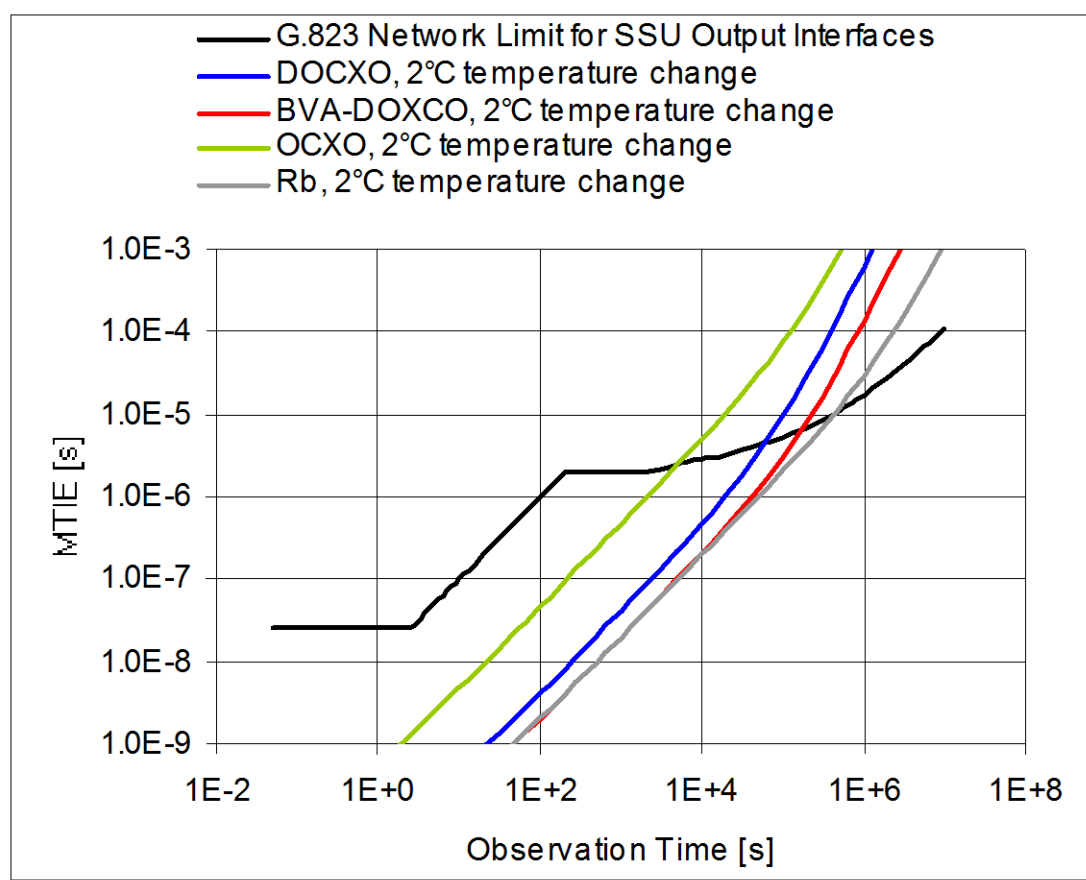3. XO Performance vs. Telecom Requirements



Frequency Holdover Autonomy

How long can the SSU stay in holdover mode until the MTIE hits the Network Limit for PRC-traceable SSU outputs (G.823)?





Frequency Holdover Autonomy

Holdover autonomy for different oscillator types and for different temperature conditions (temp. change during holdover):

	OCXO ¹	DOCXO ²	BVA- DOCXO ³	Rb ⁴
Const. Temp.	9 h	21 h	51 h	9 days
2°C	1.4 h	17 h	46 h	5.5 days
5°C	30 min	13 h	39 h	67 h
10°C	15 min	8.3 h	31 h	33 h

Notes: 1) OSA 8741 2) OSA 8663 3) OSA 8600 4) TNT RMO


Phase Holdover Autonomy (e.g. 1PPS)

Holdover Autonomy T of cdma2000 Base Stations

Temperature variation: $\pm 10^\circ\text{C}$

Criterion: phase-time accumulation ≤ 7 microseconds

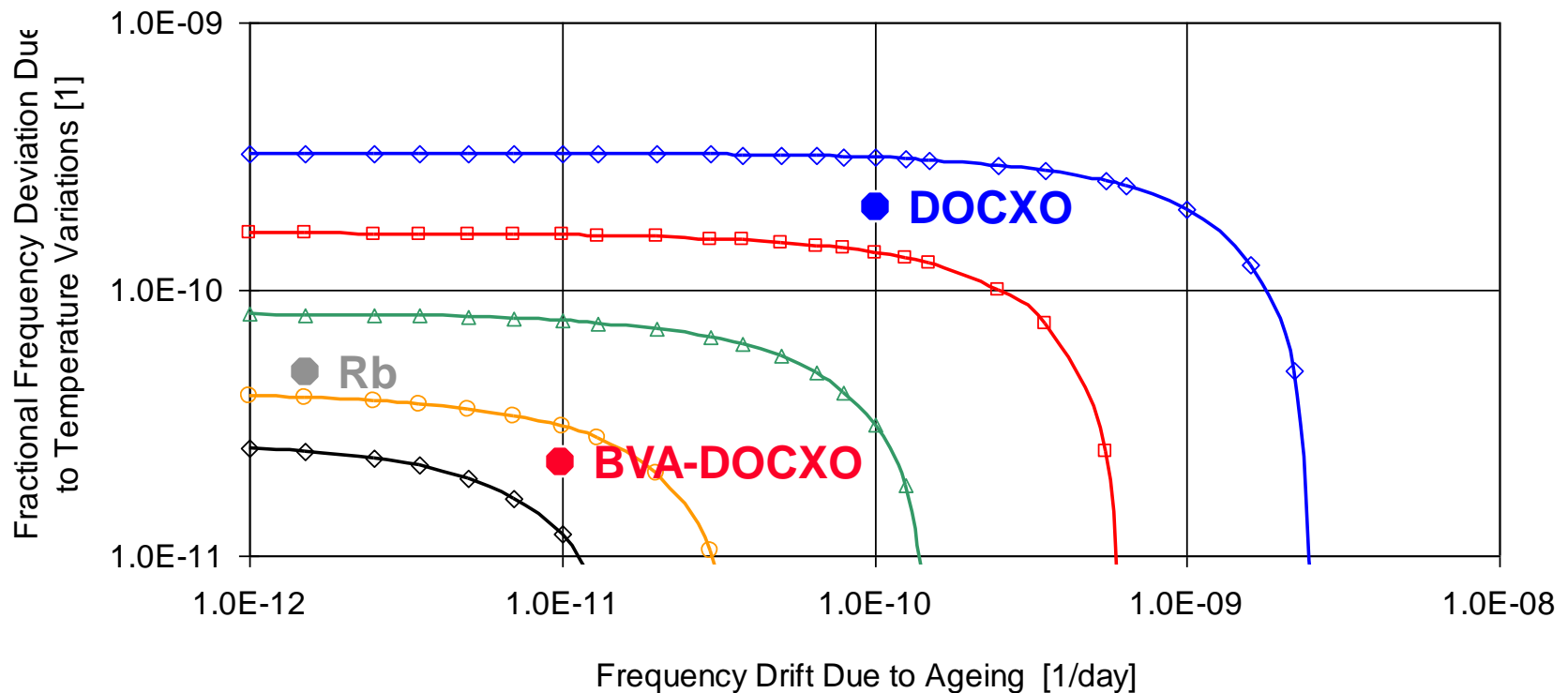—◇— T = 6 h —□— T = 12 h —△— T = 24 h —○— T = 48 h —◇— T = 72 h






4. Phase Locked Loops (PLL)



PLL: Working principle

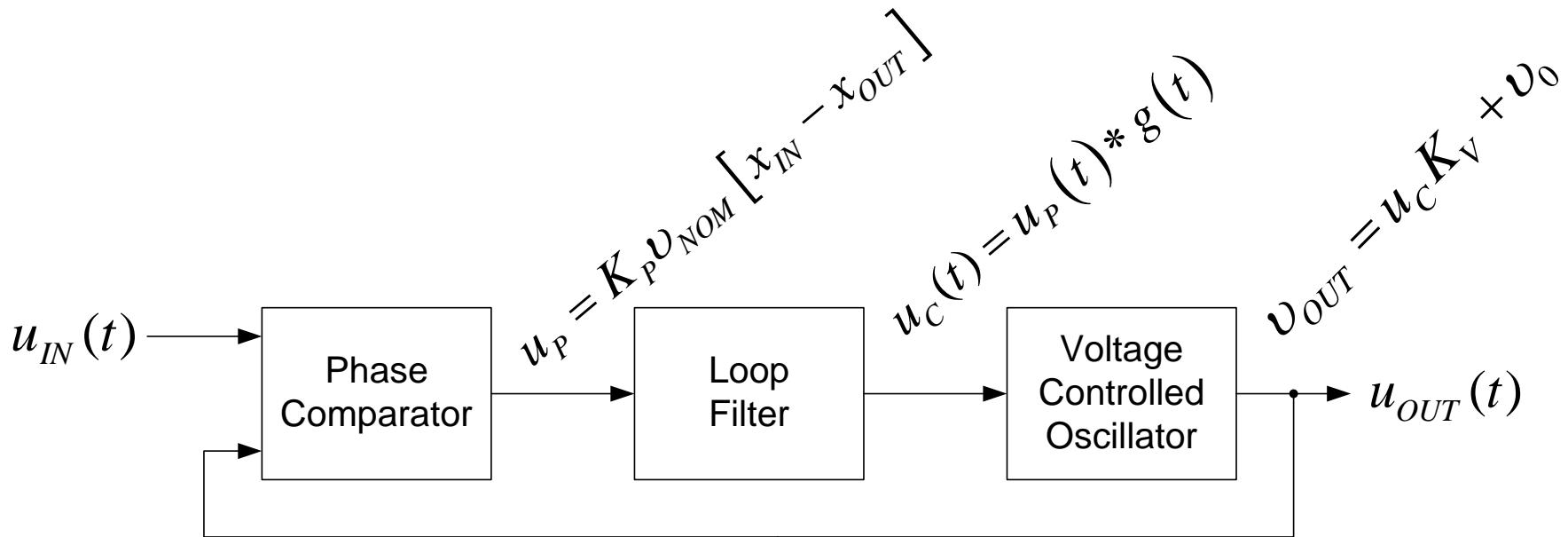

$$u_{IN}(t) = A \cdot \sin \left\{ 2\pi \nu_{NOM} \left[t + x_{IN}(t) \right] \right\} = A \cdot \sin \left\{ 2\pi \nu_{IN}(t) + \varphi_{0,IN} \right\}$$


$$u_{OUT}(t) = A \cdot \sin \left\{ 2\pi \nu_{NOM} \left[t + x_{OUT}(t) \right] \right\} = A \cdot \sin \left\{ 2\pi \nu_{OUT}(t) + \varphi_{0,OUT} \right\}$$



Phase-time deviation $x(t)$

nominal signal = $\sin \{2\pi\nu_{NOM}t\}$

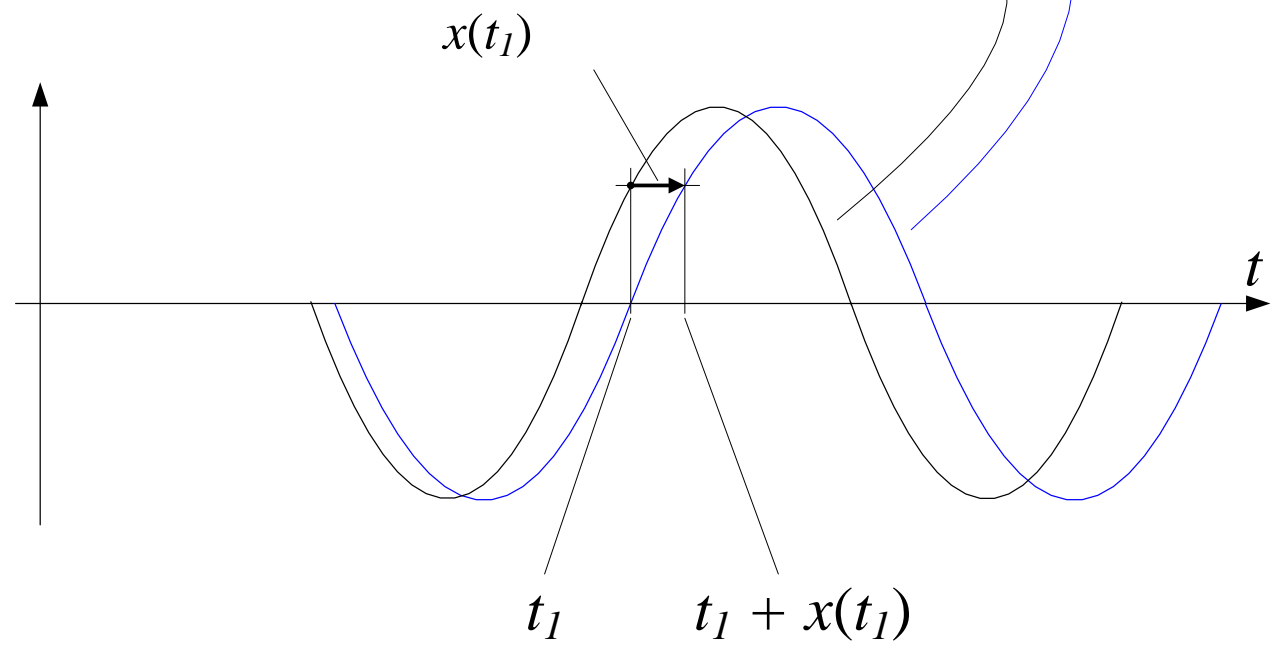actual signal = $\sin \{2\pi\nu_{NOM} [t + x(t)]\}$





PLL: Transfert function


$$u_{OUT}(t) = u_{IN}(t) * h(t)$$

$$U_{IN}(s) = U_{OUT}(s) \cdot H(s)$$

where $h(t)$ = impulse response

$$H(s) = \text{transfer function} = \text{Laplace}\{h(t)\}$$

$$20\log|H(j2\pi f)| \text{ [dB]}$$

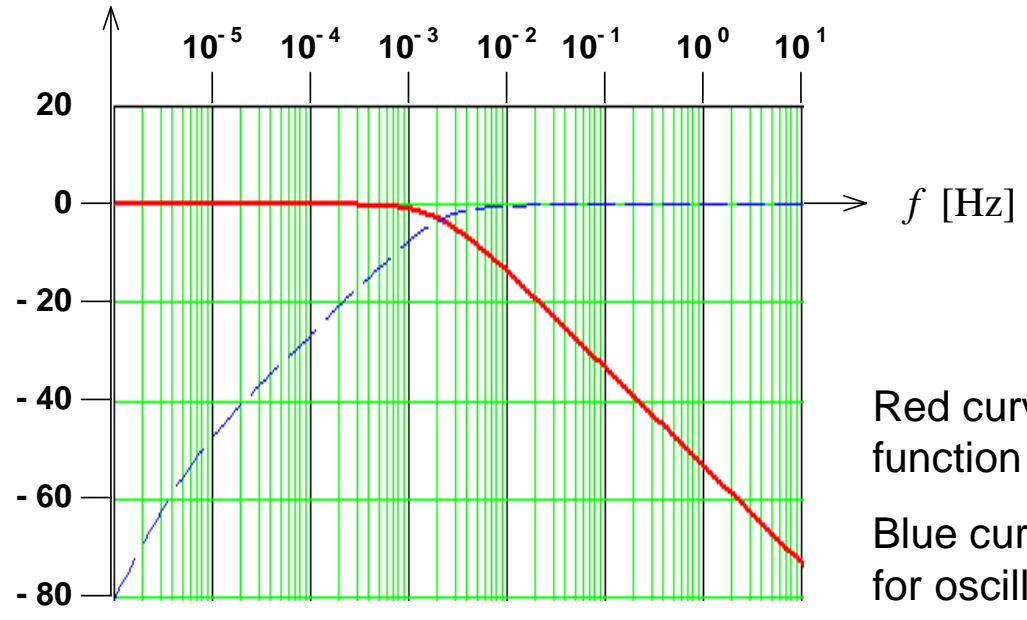


Red curve = PLL transfer function

Blue curve = transfer function for oscillator noise





PLL: Jitter filtering

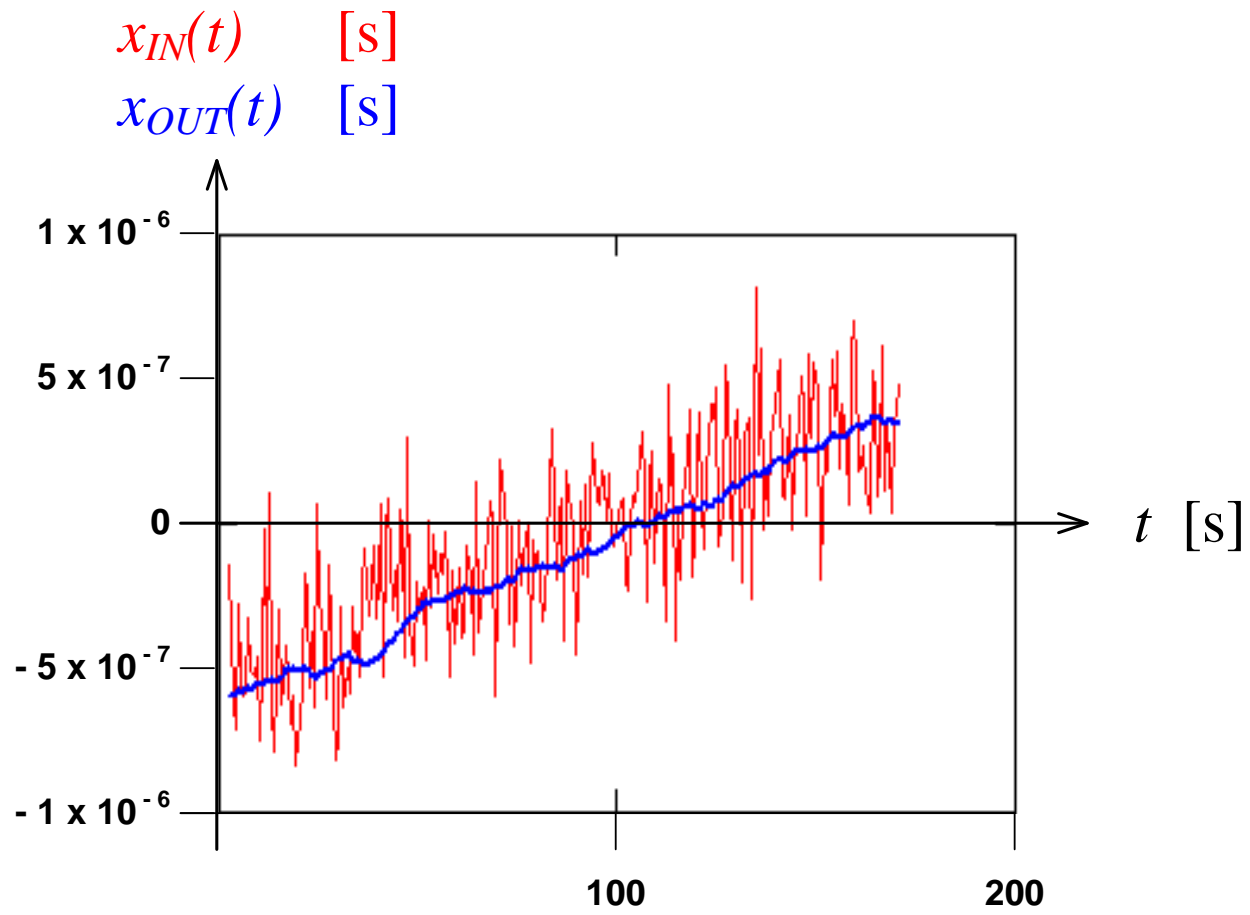



PLL with Direct Digital Synthesis

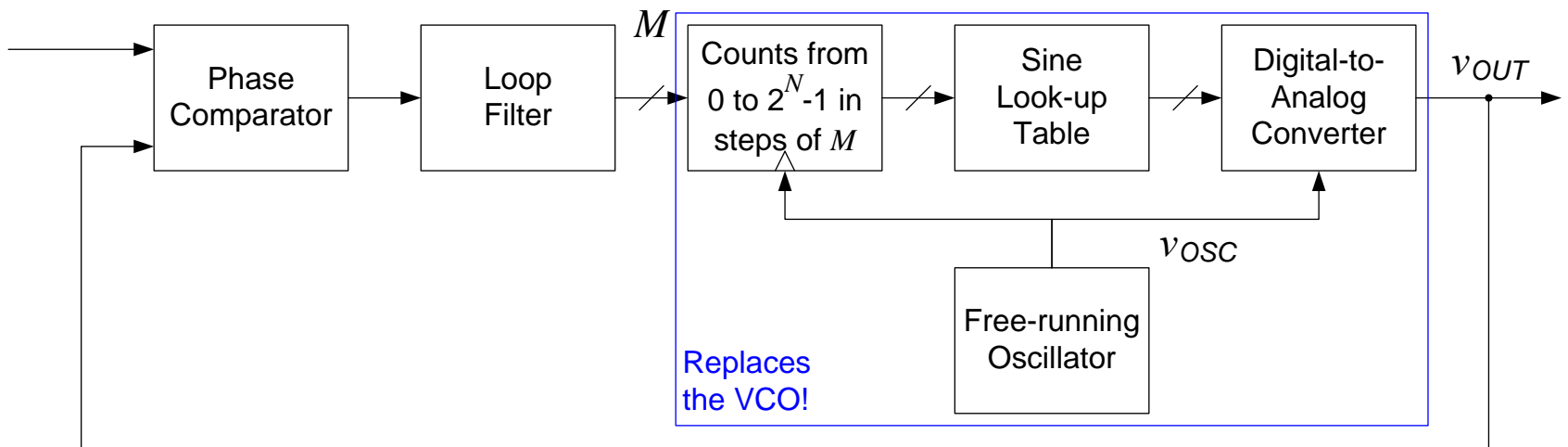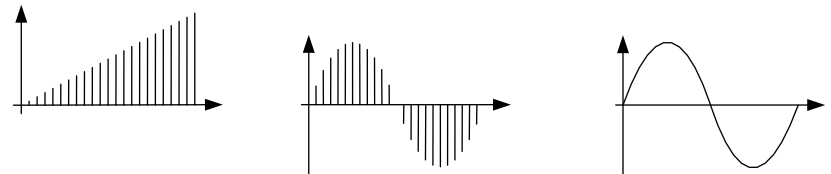

$$\nu_{OUT} = \frac{M}{2^N} \nu_{OSC}$$

where M = output of the digital loop filter (integer)

N = size of the counter in bits (integer)

ν_{OUT} = frequency of output signal $u_{OUT}(t)$

ν_{OSC} = free-run frequency of the oscillator



PLL with VCO and with DDS compared

	Pros	Cons
PLL with VCO	<ul style="list-style-type: none">•Very low phase noise	<ul style="list-style-type: none">•PLL's pull-in range depends on VCO's pulling range•Requires VCO
PLL with DDS	<ul style="list-style-type: none">•Configurable pull-in range•Requires only free-running oscillator	<ul style="list-style-type: none">•Some quantization phase noise



OSCILLOQUARTZ

SWATCH GROUP  ELECTRONIC SYSTEMS

Thank you